

Aliah University
Department of Electrical Engineering
B. Tech. III sem. Examination March -2021


Sub: Circuit Theory & Networks
Full Marks: 80

Code- EENUGOE01
Duration: 3 hrs


Instruction: 1. Write from your own understanding in your own words; don't simply copy from website/notes/books etc.
2. Avoid mixing-up the answers of different groups.

Group-A
(Answer any five questions: 5 X 8 = 40 Marks)

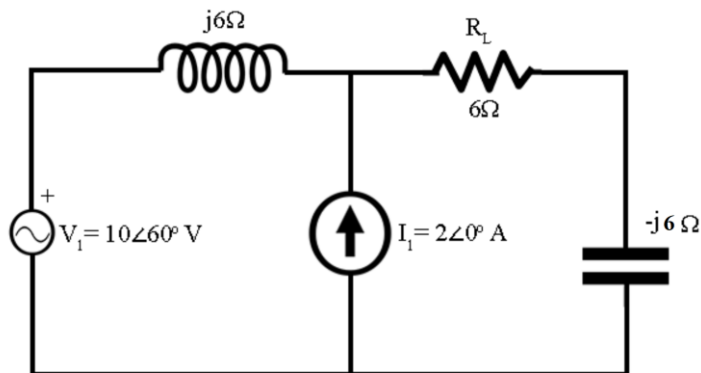
1. Find the current in the resistor R_L using the principle of superposition in Fig. below. [8]



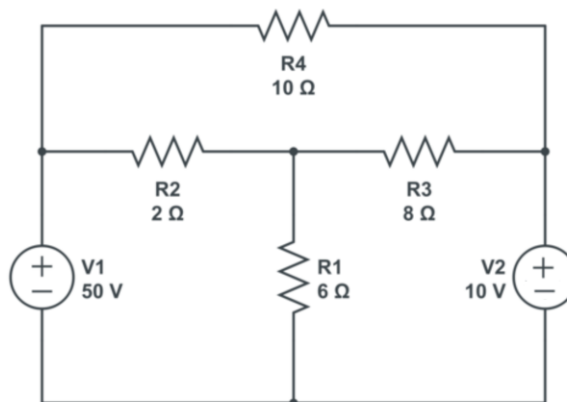
2. (a) Distinguish between unilateral and bilateral circuit elements. [2]
(b) Determine current through resistor R_2 using mesh analysis shown in Fig. below. [6]



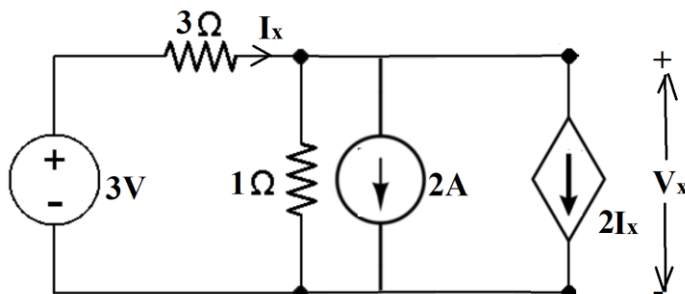
3. (a) State Thevenin's theorem. [3]
(b) Find V_x and I_x for the circuit shown in Fig. below. [5]



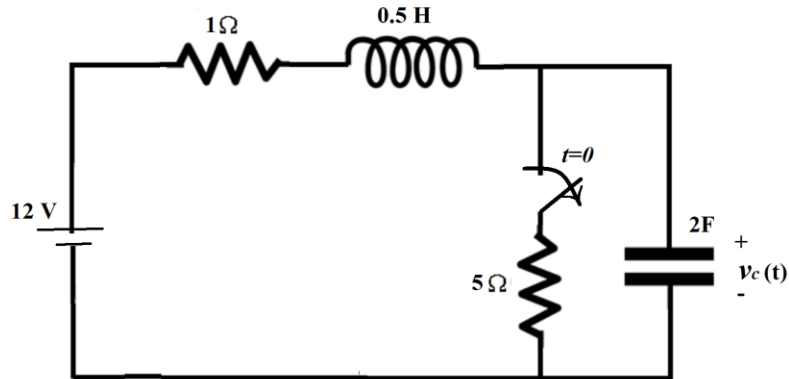
4. (a) Find Laplace transform of $f(t) = e^{-3t} \cos 5t$ [2]
 (b) Consider the circuit shown in Fig. below. The switch was closed for a very long time and at time $t = 0$, the switch is opened. Find the expression of $v_c(t)$ for $t > 0$. [6]



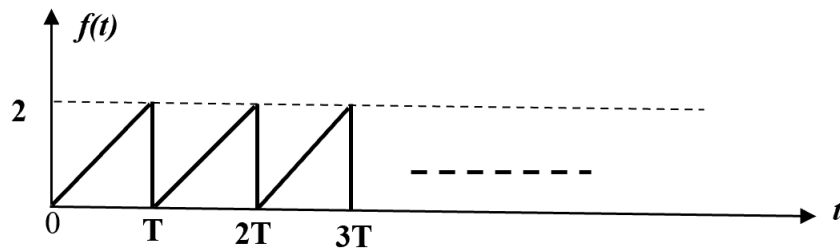5. (a) Prove that $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$. [3]
 (b) Find the Laplace transform of the signal shown in Fig. below. [5]



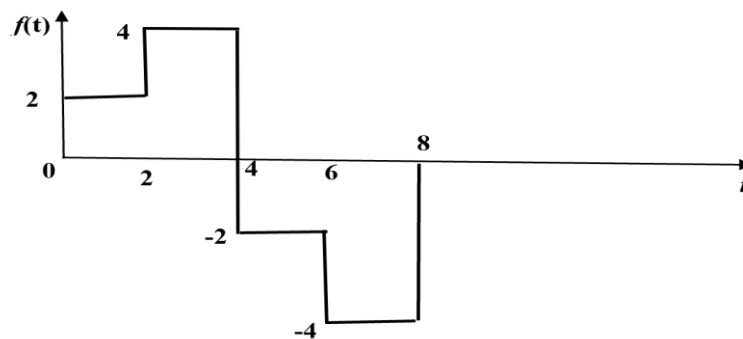6. (a) Find inverse Laplace transform of $F(s) = \frac{(s+2)}{(s+1)^2(s+3)}$. [4]
 (b) Consider the signal shown in Fig. below. Represent the signal in terms of unit step function. [4]




Group-B
(Answer any Five: 5 X 8 = 40 Marks)

7. (a) Derive the condition for reciprocity and symmetry for T-parameters. [3]
 (b) Derive h-parameters in terms of Y-parameters and T-parameters in terms of h-parameters. [5]


8. Find the open circuit impedance parameters for the given circuit.

[8]

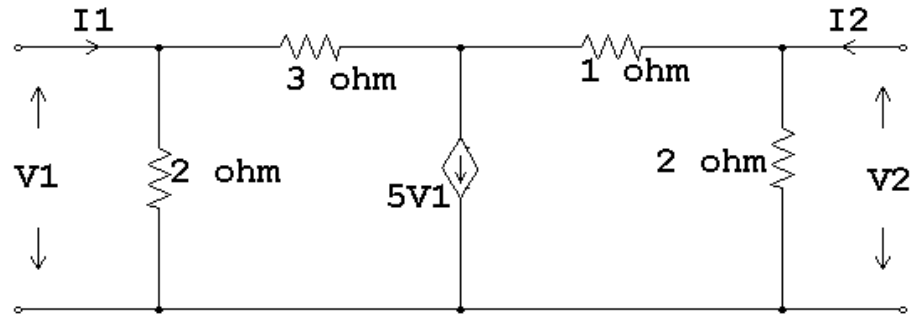


9. (a) The hybrid parameters of the network 'N' shown in figure are: $h_{11} = 1 \Omega$, $h_{12} = 1$, $h_{21} = -4$, $h_{22} = 5 \Omega$. Determine the supply voltage V_s , if the power dissipated in the load resistor R_L ($= 8 \Omega$) is 30 W and $R_S = 2 \Omega$.

[4]

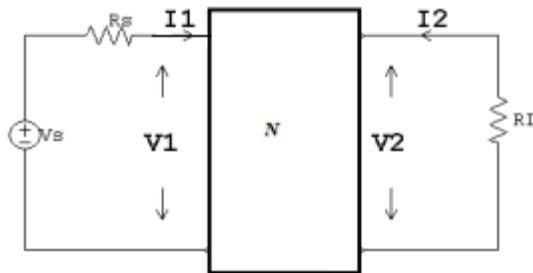

- (b) Find the transmission parameters for the network:

[4]

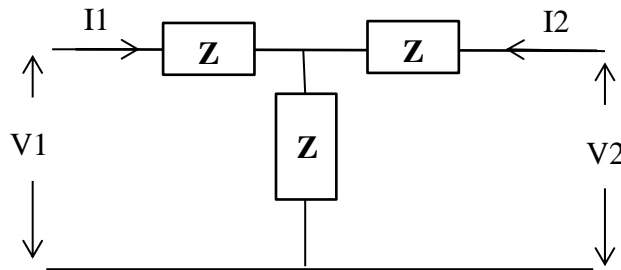

10. A 3-phase, 4-wire system having a 230 V phase voltage has the following loads connected between the respective lines & neutral: $Z_R = 15 \angle 30^\circ \Omega$, $Z_Y = 15 \angle 45^\circ \Omega$, & $Z_B = 15 \angle 60^\circ \Omega$. Calculate the current in the neutral wire and power taken by each load.
11. A symmetrical 3-phase, 420 V system supplies a star-connected load of $Z_R = 8 \angle 30^\circ \Omega$, $Z_Y = 10 \angle 45^\circ \Omega$, & $Z_B = 12 \angle 50^\circ \Omega$. Assuming the neutral of the supply is earthed, calculate the voltage of the star point to earth.
12. Take an arbitrary network of your choice (minimum 4 nodes). Draw its oriented graph and select a tree. From thereon express the following:
- Relation between incidence matrix and branch current matrix
 - Relation between tie-set matrix and branch voltage matrix.
 - Relation among branch currents matrix, fundamental loop currents matrix and tie-set matrix.