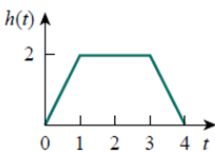


**Aliah University**  
**Electrical Engineering Department**  
**B.Tech 3<sup>rd</sup> Sem Online Examination 2022 ( Regular + Supplementary)**  
**Subject with code: Electrical Network Analysis (EENUGPC01)(Reg+Sup)**  
**Electrical Network Analysis (EE 201) (Sup)**  
**Signals & Networks (EE 201) (Sup)**

The figures in the margin indicate full marks.

All parts of a question should be answered at one place.

**Answer all questions from Group A and any four questions from Group B:**  
**(Marks: 20+15x4=80)**

- | <b>Qu. No.</b>  | <b>Group A (4+4+12=20)</b>   | <b>Marks</b>   |
|---|--|----------------|
| <b>1.a.</b>   | Find the Laplace transform of $h(t)$ in Fig.1  | <b>4</b>       |
|  |  |                |
| Fig.1   |  |                |
| <b>1.b.</b>   | State Dirichlet's conditions for a function to be expanded as a Fourier series.  | <b>4</b>       |
| <b>1.c.</b>   | For the circuit shown in Fig. 2., (i) draw the oriented graph and write the (ii) incidence matrix, (iii) f-cutset matrix. (iv) How many trees are possible for the graph of the network? | <b>2+3+3+4</b> |

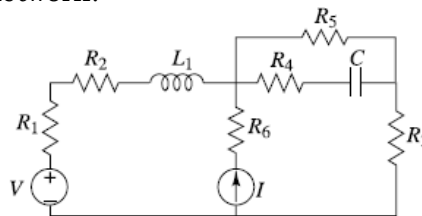


Fig. 2.

- | <b>Qu. No.</b> | <b>Group-B(15x4=60)</b>   | <b>Marks</b> |
|----------------|---|--------------|
| <b>2.</b>      | What is super node in electrical circuit? In the network shown in Fig. 3., find the node voltages $V_1$ and $V_2$ and current in the branch with the resistor $4\Omega$ . | <b>2+13</b>  |

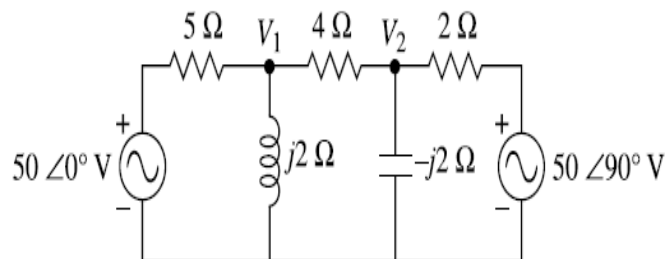


Fig. 3.

Qu. No.		Marks
3. a.	Write differences between independent and dependent voltage/current source.	4
3.b.	Find the current through $6\Omega$ resistor shown in Fig. 4. using the mesh analysis. Here, voltage source is $10\angle 60^\circ V$ and current source is $2\angle 0^\circ A$ .	11

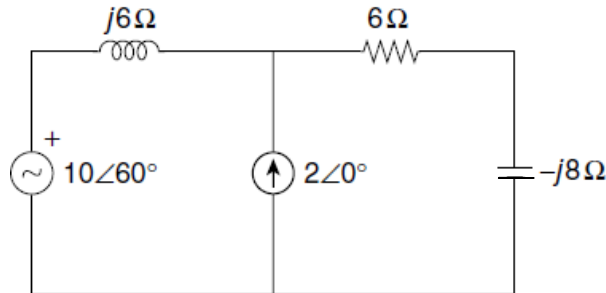


Fig. 4.

4. State Thevenin's Theorem. Find the current in the  $(5+j4)\Omega$  impedance connected between A and B in the circuit shown in Fig. 5. using Thevenin's theorem. 3+12

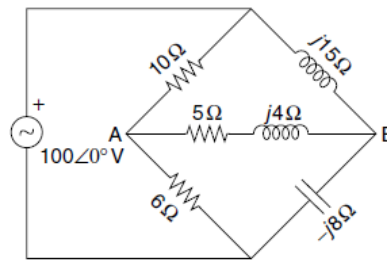


Fig. 5.

5. a. Evaluate Laplace Transform of  $\sin^3(t)$  5  
 5. b. A series  $R-L$  circuit shown in Fig. 6. experiences an exponential voltage  $v = 10e^{-100t} V$  after closing the switch at  $t = 0$ . Find the expression for current  $i(t)$  using Laplace transform. Assume zero initial inductor current before switching. 10

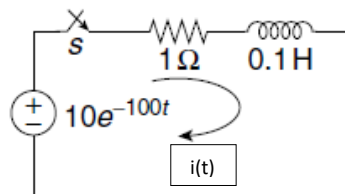


Fig. 6.

6. Why do we need two port network? For the network, shown in Fig. 7., find  $Z$ -parameters. 3+12

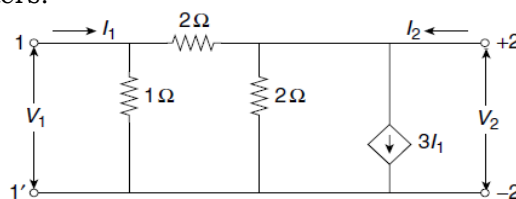


Fig. 7.

-----X-----