

ALIAH UNIVERSITY

B.Tech End Semester (Odd) Examinations 2021

Subject- Basic Electronics Engineering (ESC ECEUGES01)

CSE , CEN, MEN 1st Year 1st SEM

Full Marks : 80

Time-3 hrs

(Answer any five)

1. (i) Briefly explain the formation of energy band in solid state materials.
(ii) Distinguish between insulator, semiconductor and metal on the basis of energy band diagram.
(iii) Differentiate between intrinsic and extrinsic semiconductor. (6+6+4)
2. (i) How is an n-type semiconductor formed?
(ii) Explain the Fermi-Dirac distribution function with graphical interpretation.
(iii) Show that in n-type semiconductor the Fermi level energy E_F is close to the conduction band edge E_c of the band diagram. (3+8+5)
3. (i) Show that equilibrium concentrations of electrons (n_0) and holes (p_0) in a semiconductor can be expressed as :- (symbols have usual meaning)
(a) $n_0 = N_c e^{-\left(\frac{E_c - E_F}{KT}\right)}$ (b) $p_0 = N_v e^{-\left(\frac{E_F - E_v}{KT}\right)}$
(ii) Show that the product of electron and hole concentrations under equilibrium is constant and can be expressed as :- $n_0 p_0 = n_i^2$. (symbols have usual meaning) (6+6+4)
4. (i) Explain the formation of the depletion region and barrier potential V_0 in a p-n junction diode.
(ii) Show that the barrier potential can be expressed as :- (symbols have usual meaning)
$$V_0 = \frac{KT}{q} \ln \frac{N_a N_d}{n_i^2}$$
 (4+4+8)
5. (i) Explain the operation of the clipper circuit with the input shown in **Fig. 1**, assuming the diode as ideal diode.
(ii) Find out the changes in the output voltage waveform if the diode is a real one with cut-in voltage v_γ and diode dynamic resistance r_d after estimating the output voltage expression.
(iii) Draw and explain the output of the circuit shown in **Fig. 2** for the given input. (5+5+6)

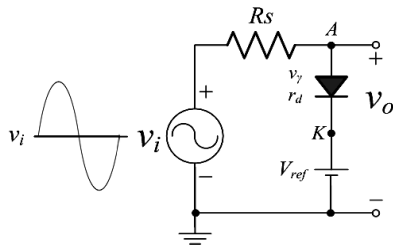


Fig. 1

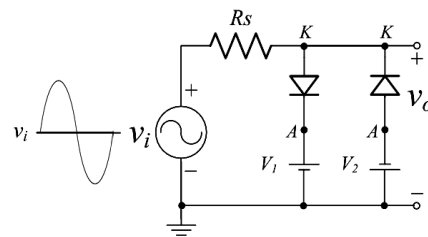


Fig. 2

6. (i) Explain the operation of full wave rectifier circuit with bridge network with a output waveform diagram.
(ii) Show that the output DC voltage (V_{dc}) and ripple factor (Γ) of full wave rectifier output is
(a) $V_{dc} = 0.636 V_m$ (b) $\Gamma = 48.3 \%$

(4+5+3+4)

7. (i) Explain different current components in a p-n-p transistor in active region with a suitable diagram.
(ii) Establish the relation between current amplification factors α and β . (6+4+6)
(iii) Briefly explain the CB, CE and CC mode operation in a transistor.
8. (i) Draw the output characteristics of CE amplifier and explain it.
(ii) With neat diagram explain the fixed bias circuit of CE amplifier.
(iii) Draw the DC load line and Q-points of the CE amplifier circuit. Why is the Q-point need to remain in the middle of the load line? (4+4+6+2)
9. Find the input-output relation of the circuits shown in Fig. 3 and Fig. 4. (8+8)

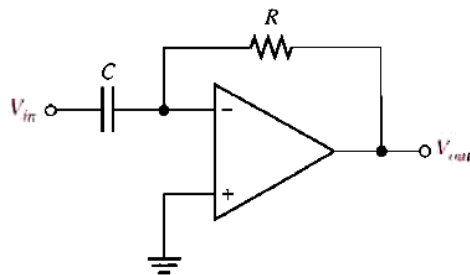


Fig. 3

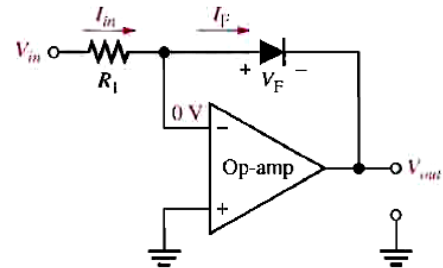


Fig. 4

-----END-----