

**B. Tech Examination 2021-22**  
**Computer Science and Engineering**  
**(Odd Semester Regular & Supplementary)**  
**Digital Logic ( CSEUGPC02 )**

**Full Marks: 80**

**Time : 3.00 Hrs**

(Answer any 8 questions.)

Symbols have their usual meaning.

1. How do you compare the following numbers? 2x5=10  
 a)  $(1.10)_2$ ,  
 b)  $(1.10)_5$ ,  
 c)  $(1.10)_8$ ,  
 d)  $(1.10)_{10}$ ,  
 e)  $(1.10)_{16}$
2. Represent the decimal number  $(-25)_{10}$  into 10  
 a) 8-bits signed magnitude form,  
 b) 8-bits signed 1's complement form,  
 c) 8-bits signed 2's complement form.
3. Perform the addition in BCD code of the two numbers 875 and 653. 10
4. Prove the equality,  $a.b + \bar{a}c = (a + c)(\bar{a} + b)$  10
5. Draw the K-MAP, solve and implement a optimum circuit of the following function 10  
 $G = \sum_m (2, 3, 4, 5, 6, 8, 9) + \sum_d (10, 11, 12, 13, 14, 15)$
6. Perform the subtraction  $(P - Q)$  in 2's complement form, where  $P = 11100101$  and  $Q = 11101101$  10
7. Design a full-subtractor using two 4:1 multiplexers. 10
8. Design a full-adder using one 3:8 decoder. 10
9. Solve the prime implicants using KMAP and draw essential prime implicants table of the following function 10  
 $G = \sum_m (1, 2, 3, 5, 6, 11, 12) + \sum_d (7, 8, 10, 14)$
10. Design a up-counter using DFF that repeats the sequence 000, 001, 010, 011, 100 in infinite loop. 10
11. Design a state machine using TFF that implements a 2-bit down-counter when input  $x=1$ , otherwise holds its current state. 10